

Build an RF Coax Shield Current Probe

w6nbc.com/slides.html




RF Probe

Stray RF in the radio shack

owenduffy.net
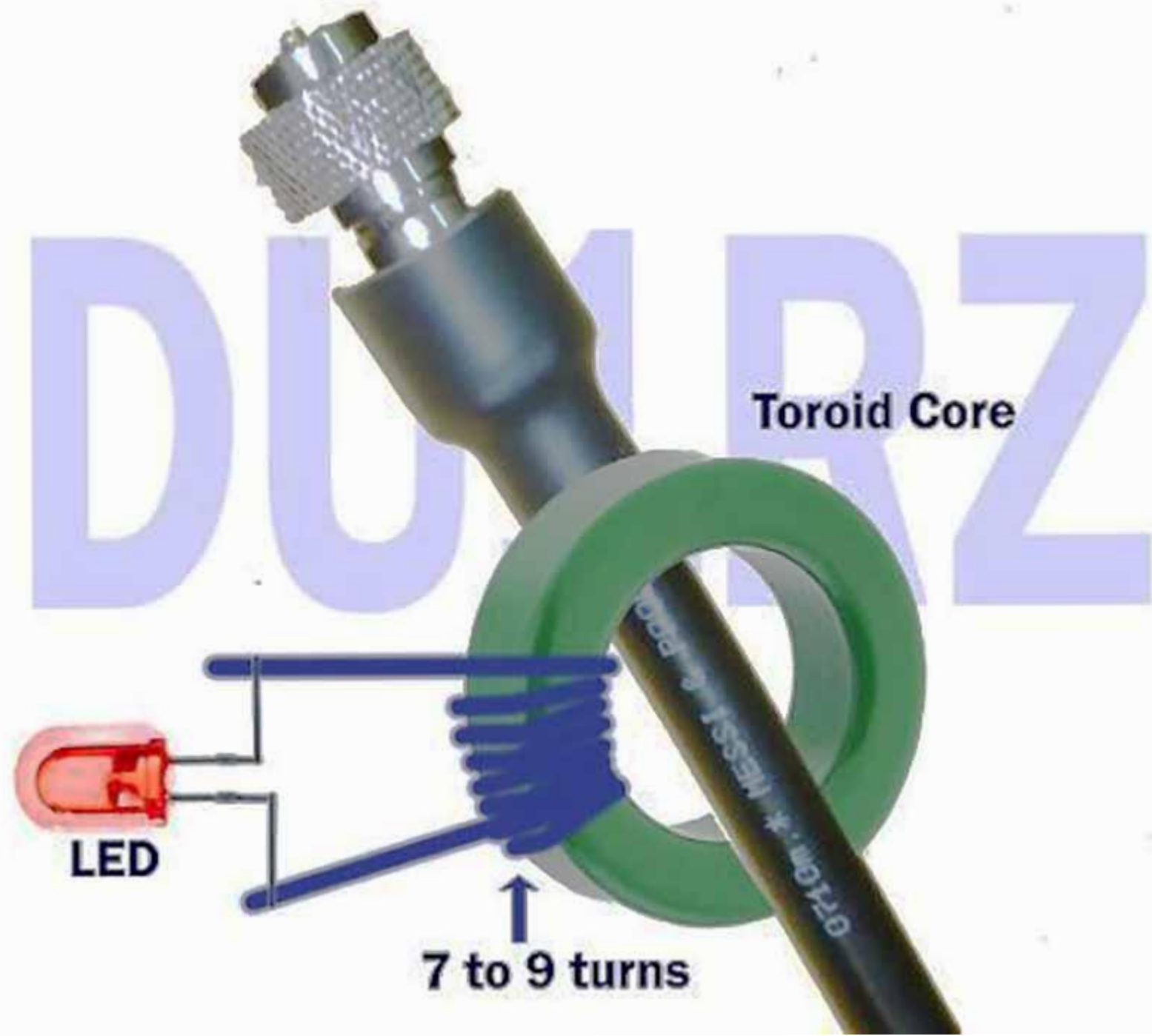
<https://owenduffy.net/module/icm/#:~:text=An%20approach%20to%20measurement%20Common%20mode%20current%20can, half%20wave%20detector%20driving%20a%20high%20impedance%20voltmeter.>







**MFJ-853H, CLAMP-ON,
MINI RF CURRENT METER, HI-PWR**

\$109.95

**Clamp-on ferrite
choke with an added
pickup coil & meter**



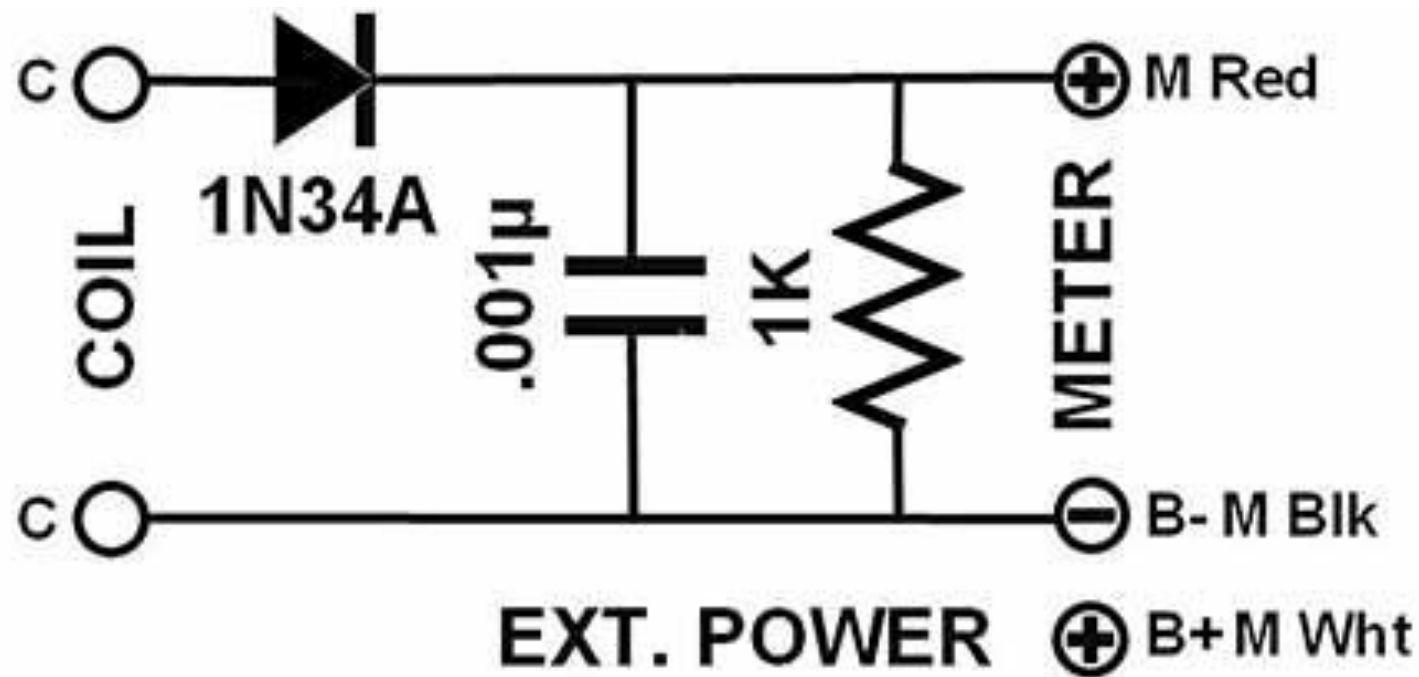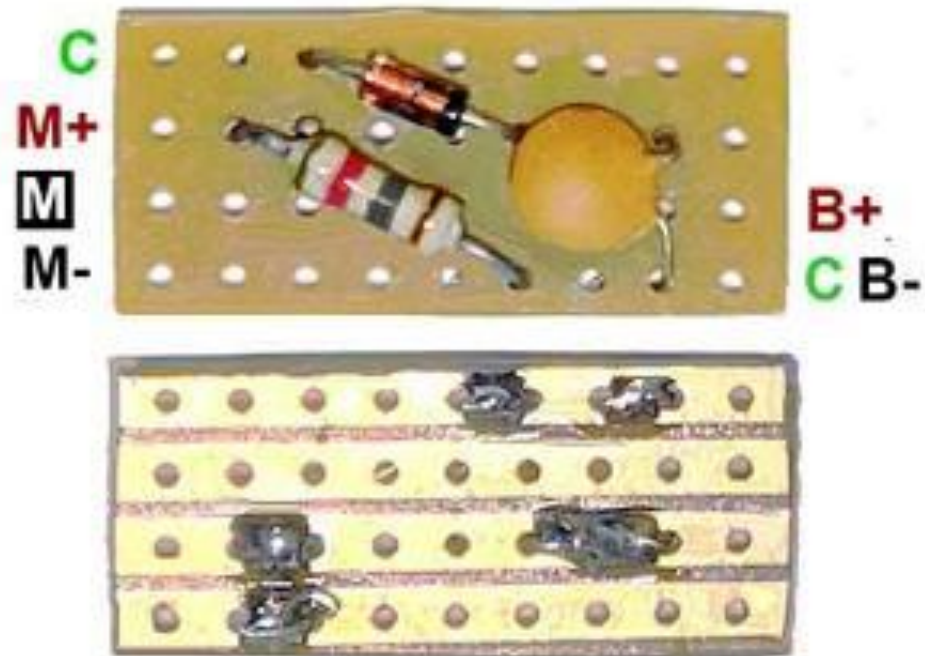**The W60EK
Version
With and
Without 3D
Printed Cover**





w6nbc.com/slides.html


Bill of Materials

w6nbc.com
/slides

1	Snap-on mix 43 Ferrite choke for RG-8, RG-213 size coax. (0.405 in.)	e.g. Fair-Rite 0443164151 snap-in, Palomar Engineers FSB43-1/2, ID=1/2" or similar
10 turns	Insulated magnet wire, AWG 24 (or smaller)	Electronic parts supplier
1	3-digit digital voltmeter, 3-wire 100V version (see text)	Amazon, <u>EBay</u> , mpja.com, Walmart, surplus electronics dealers
1	1N34 diode	Electronic parts supplier
----	100 mil linear copper strip perfboard	Electronic parts supplier
1	2 <u>cell</u> (6V) 2032 coin cell holder with cells and switch	https://www.amazon.com/dp/B092VFFCR8?psc=1&ref=ppx_yo2ov_dt_b_product_details Amazon, <u>EBay</u>
----	3M VHB Double Sided Heavy Duty Outdoor Mounting Tape or sticky squares	Local hardware store, internet
1	3D printed probe cover	<u>.stl</u> 3D printer file: <u>xxxxxx</u>

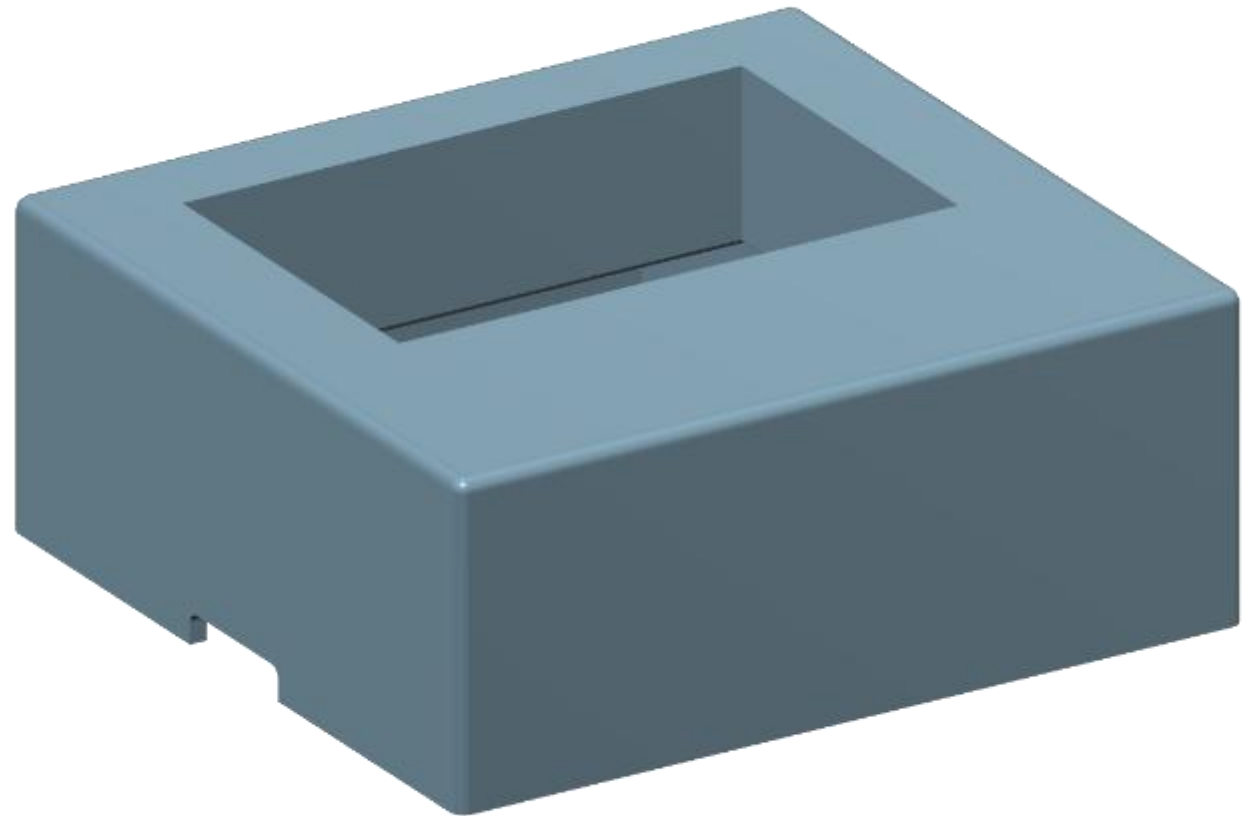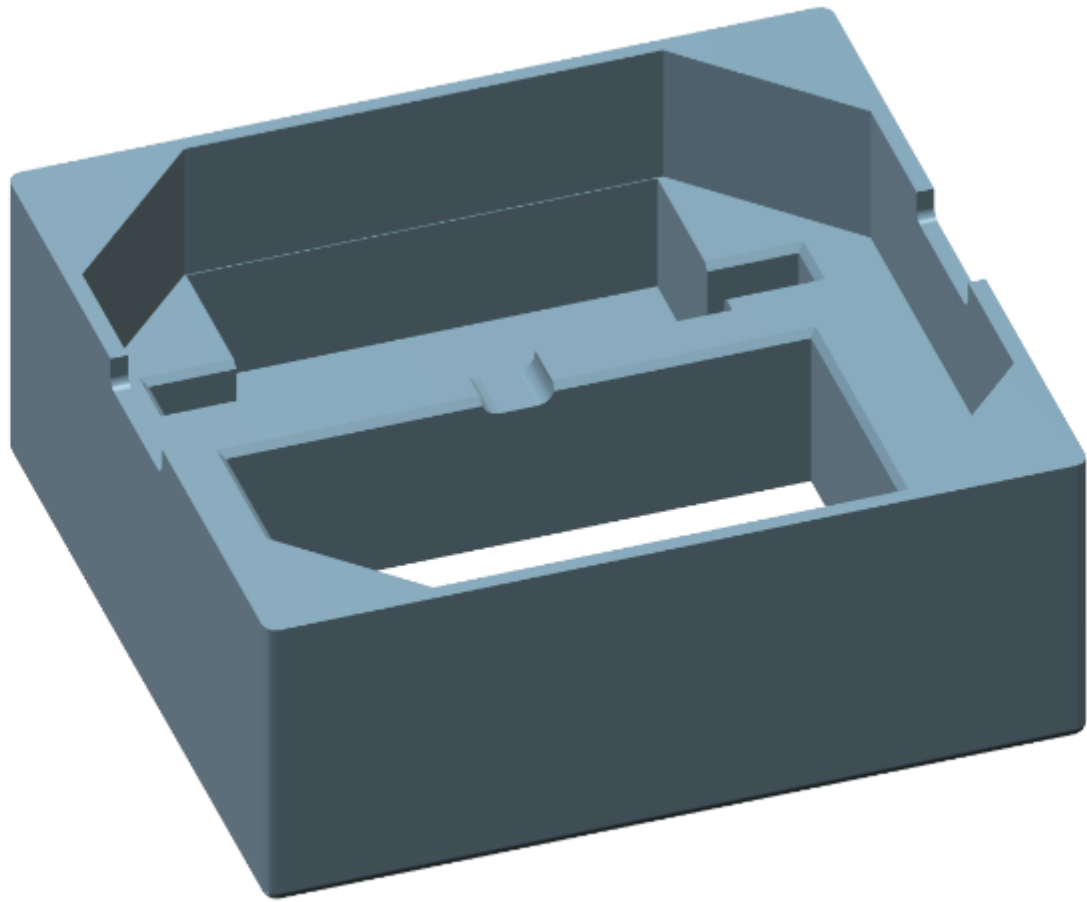

w6nbcmail@gmail.com

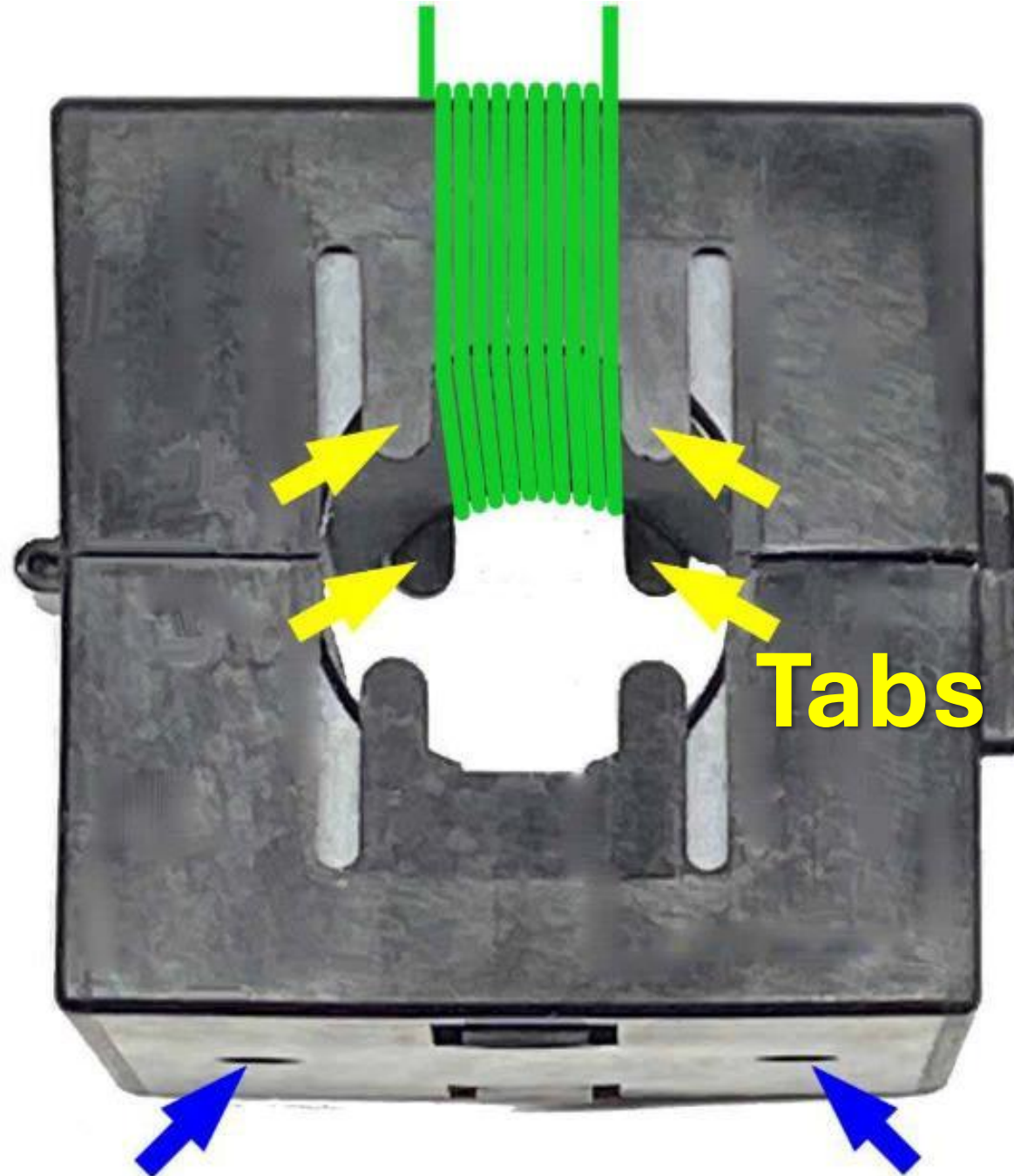


Fair-Rite
0443154151
for ½ in. coax
OK for smaller
coax

Tabs

Holes

A Better View of Baluns

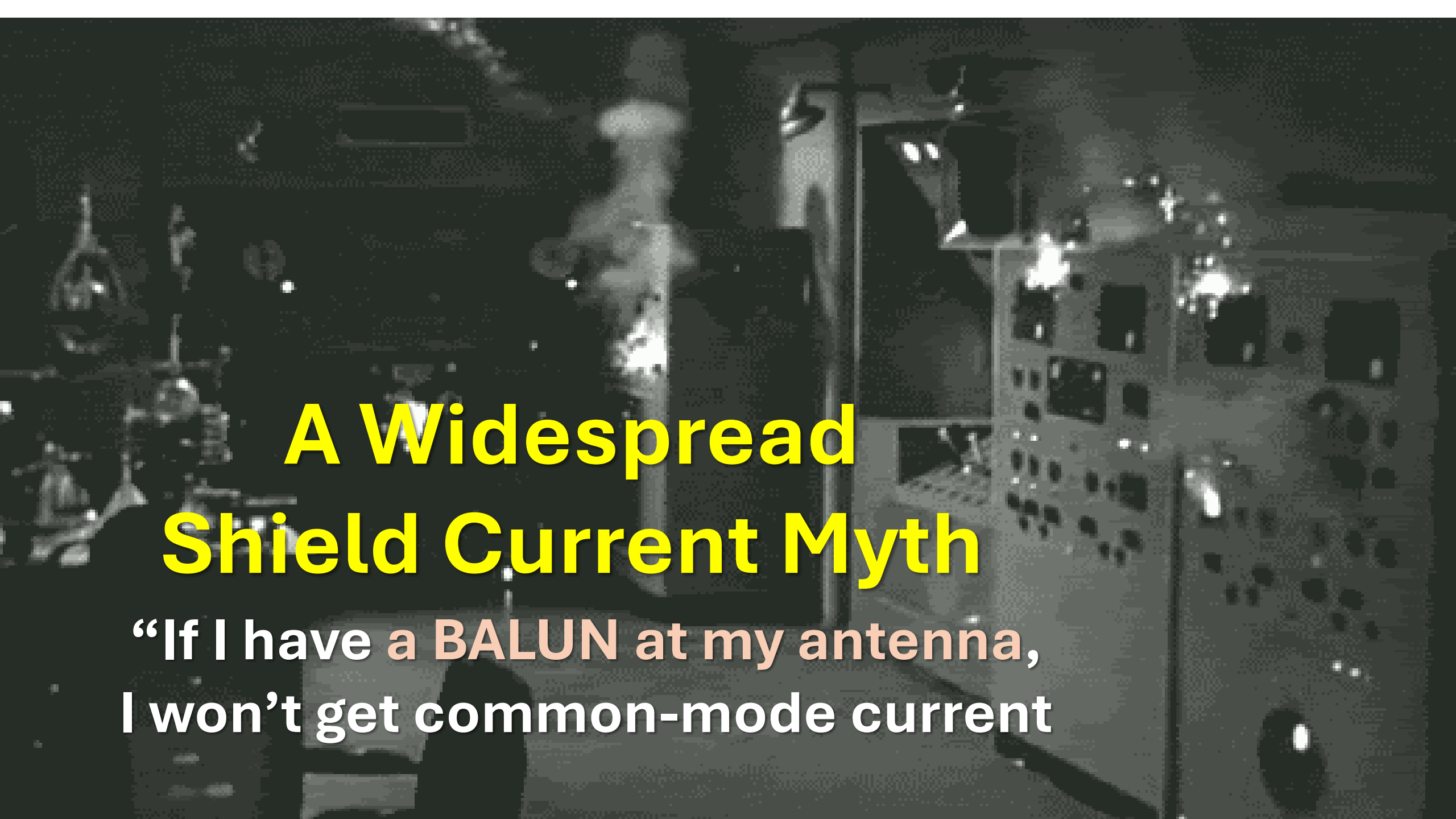


A Widespread Shield Current Myth



“If I have a **BALUN** at my antenna,
I won’t get common-mode current

The Balun is a Consequence of Skin Effect

Cross Section of Wire

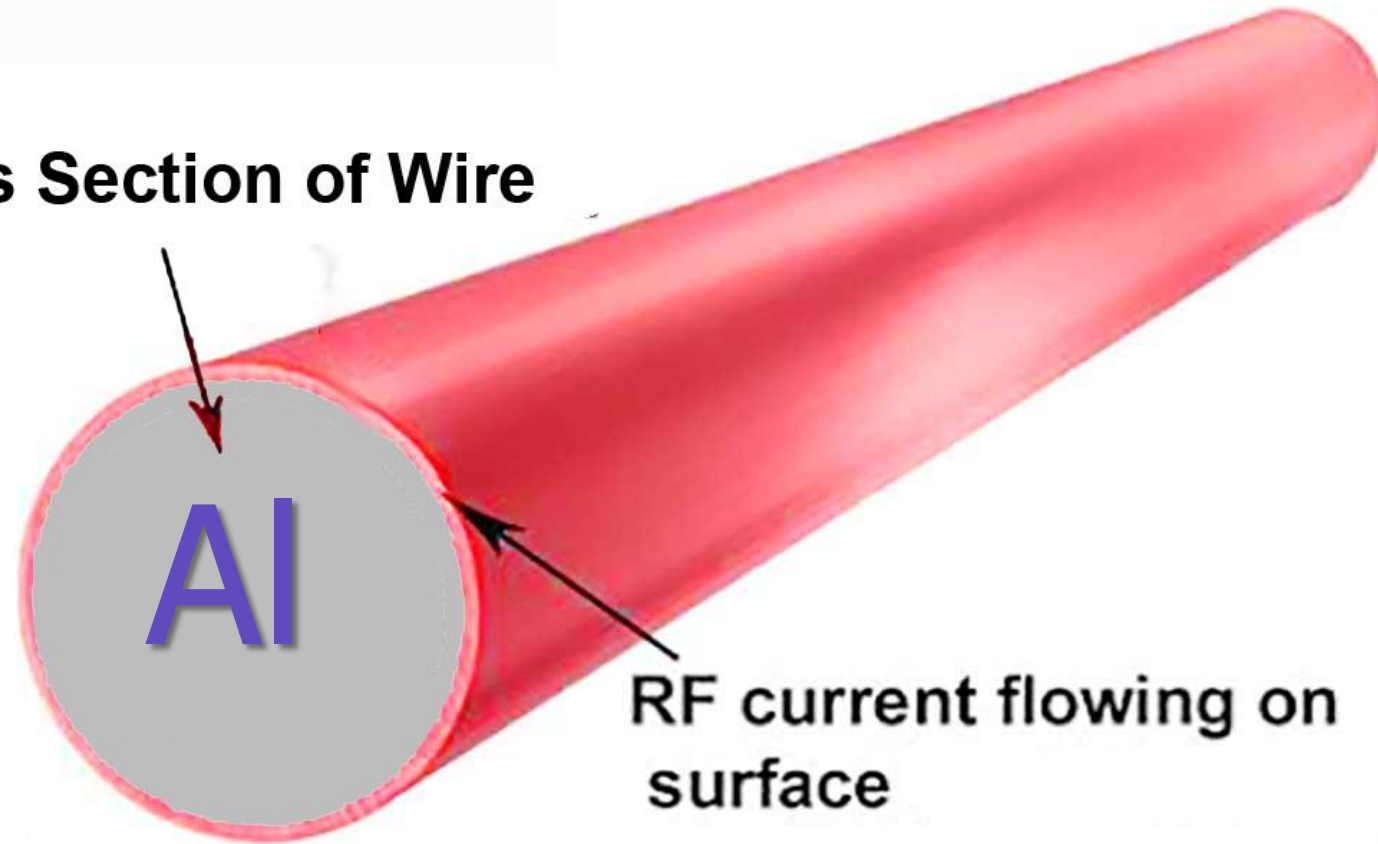



Surprise -- Coax has 3 wires

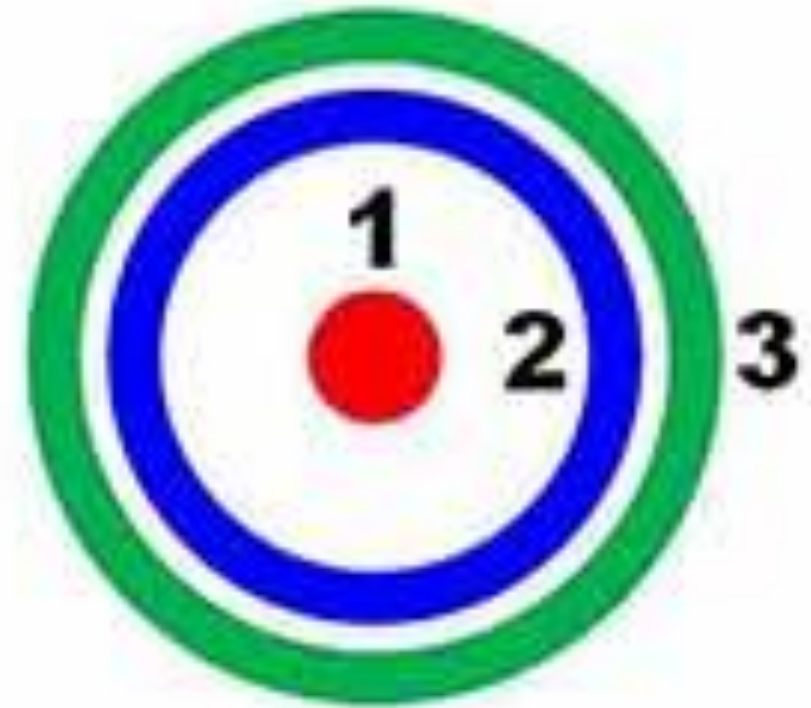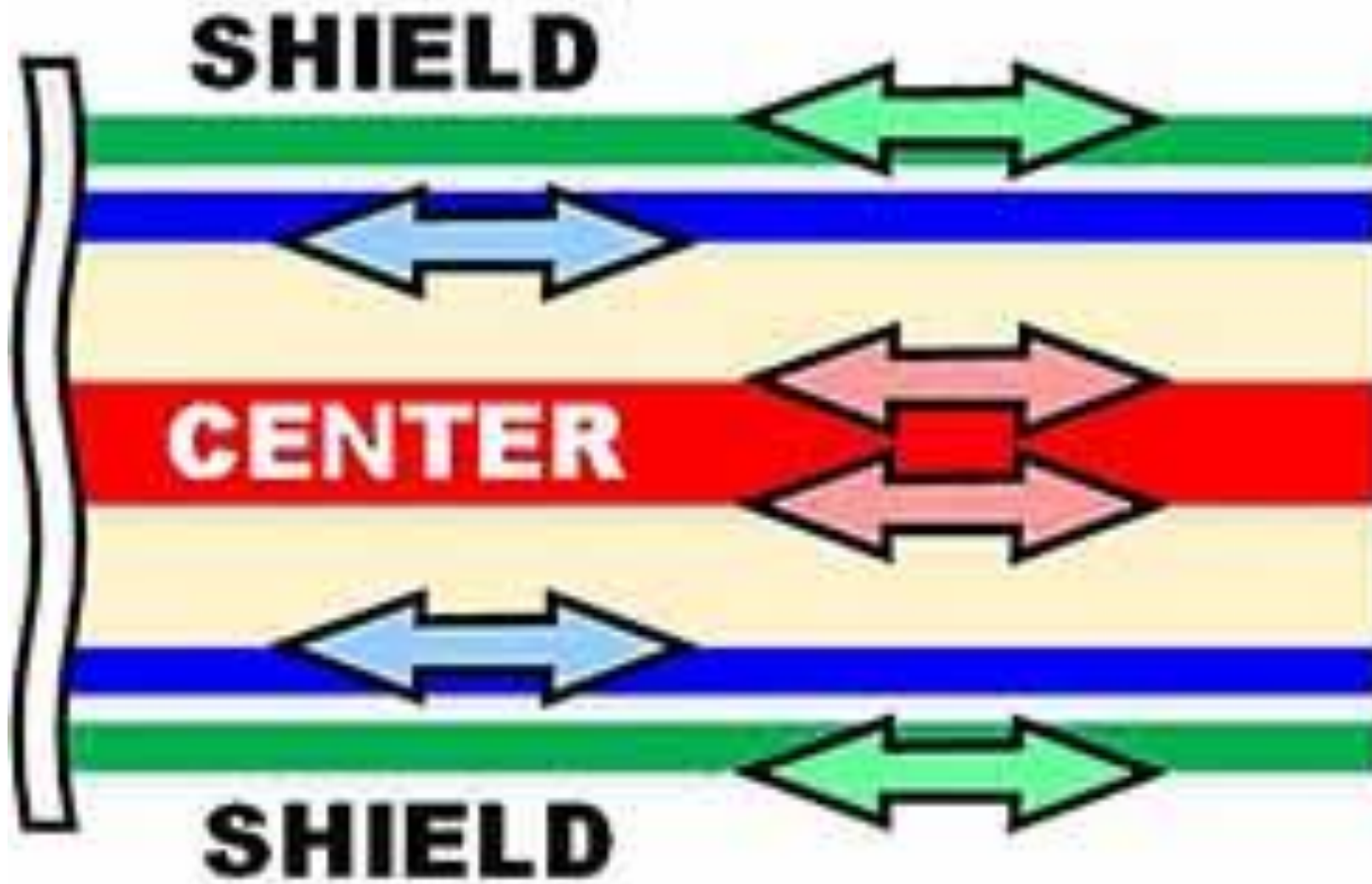


Skin forms at the end
Connects inner to outer




**Skins
continue**

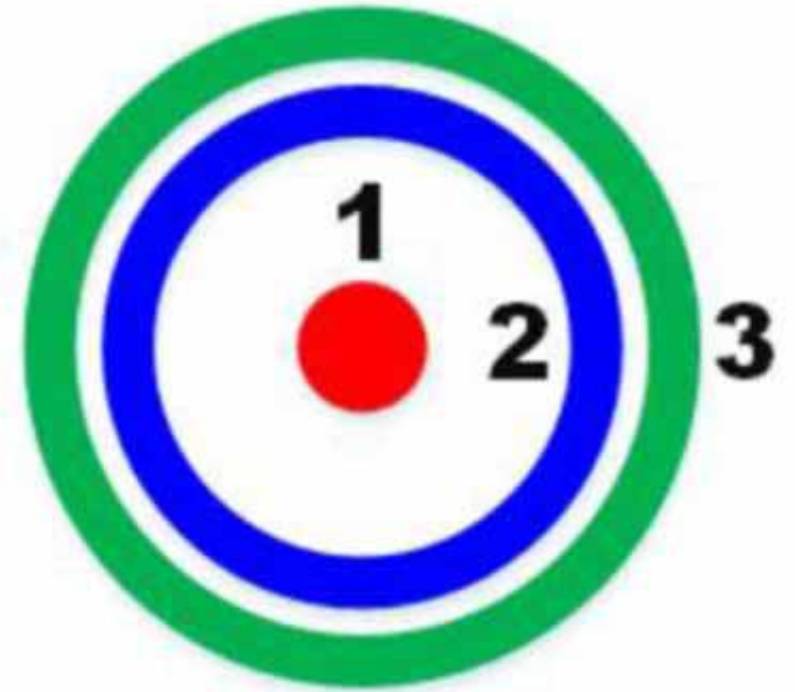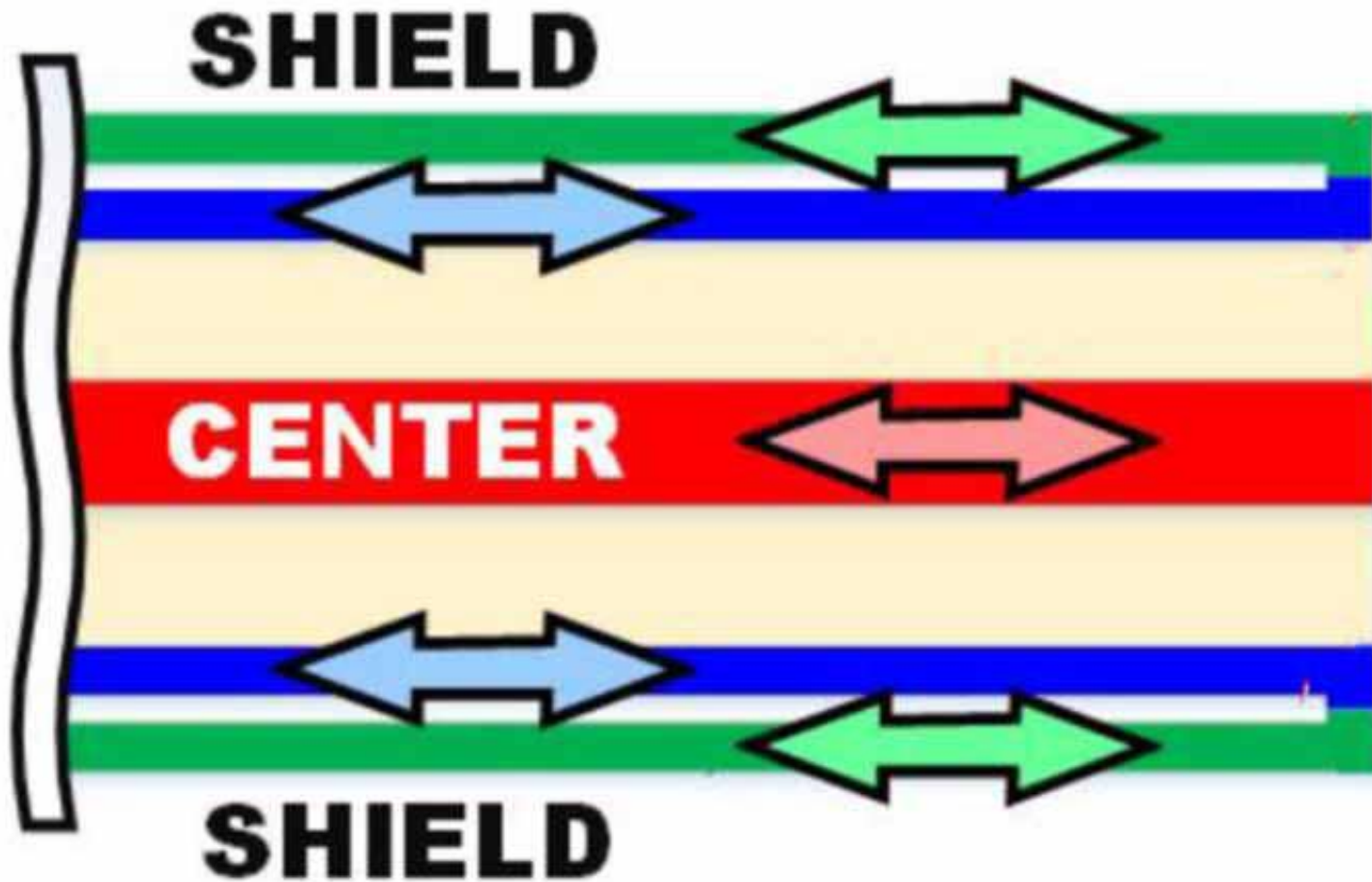

Source of Shield Current

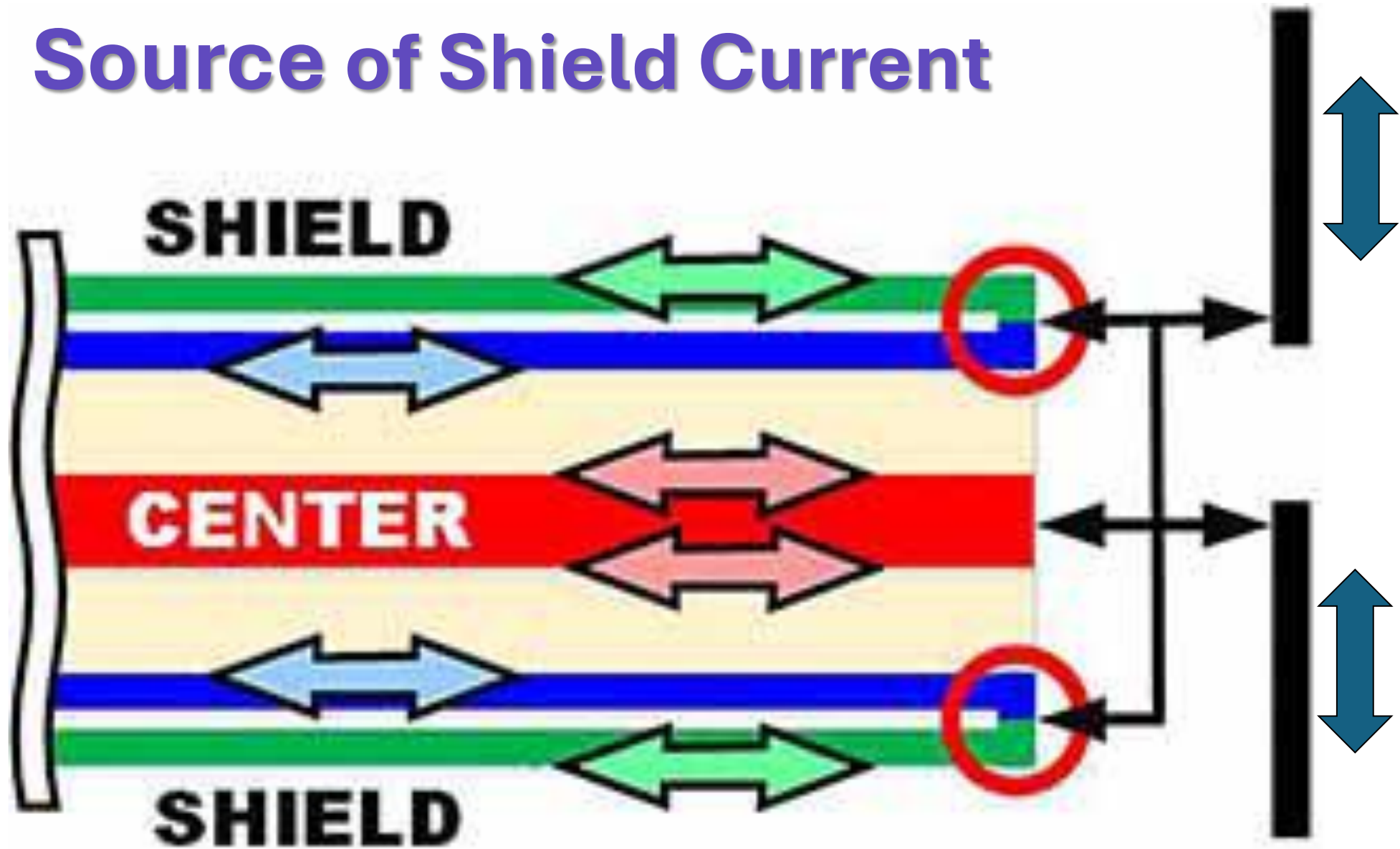

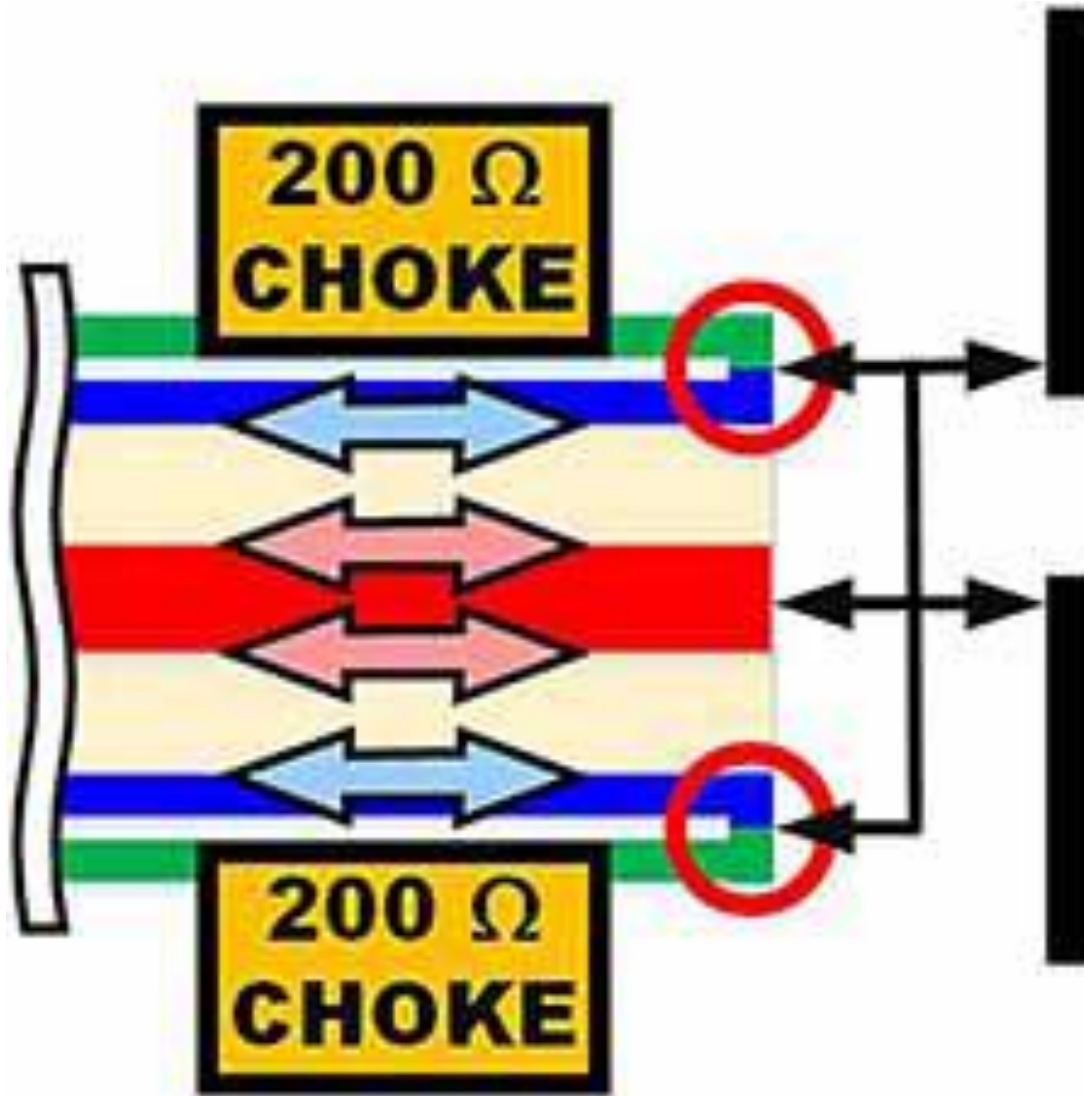

The **PRIMARY** job
of **ALL** baluns:

to "Choke Off"
to "Isolate"
the Outside Skin

i.e. "Balance"
the Inside Skins

**“Minimum” choking
impedance = 200Ω**

4 times

50Ω system impedance


OK to use more

A secondary job

**As an impedance
transformer**

4:1, 9:1

The Big Surprise

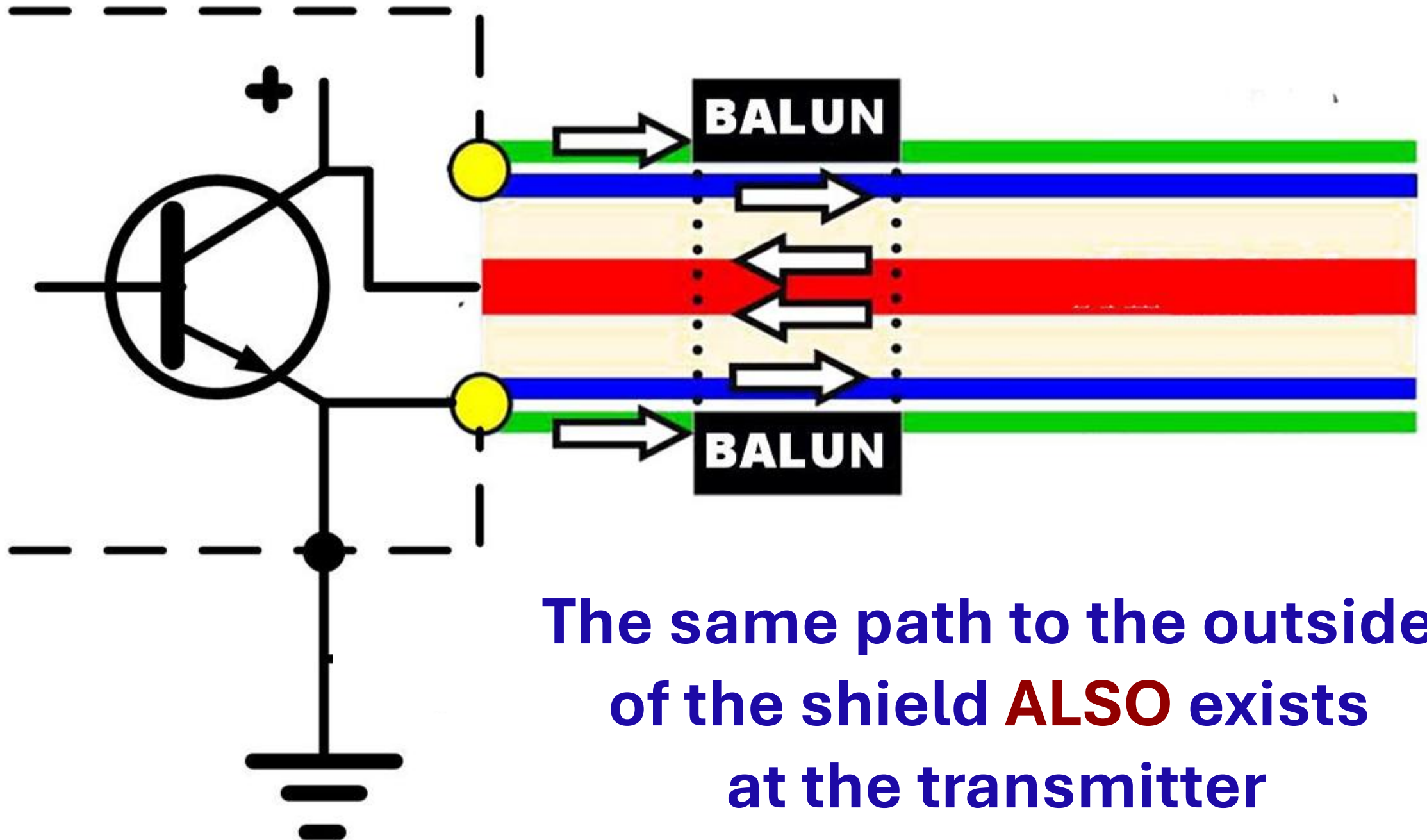

The same path to the outside
of the shield **ALSO** exists
at the transmitter

AXIOM

1. **ANY PLACE** coax ends
2. And there's a balanced source of energy


RF can get on the shield

NOT JUST AT THE ANTENNA

BOTH Antennas & Transmitters
PRIMARY Sources of Energy

NOT → Barrels, Switches
Not Sources of Energy

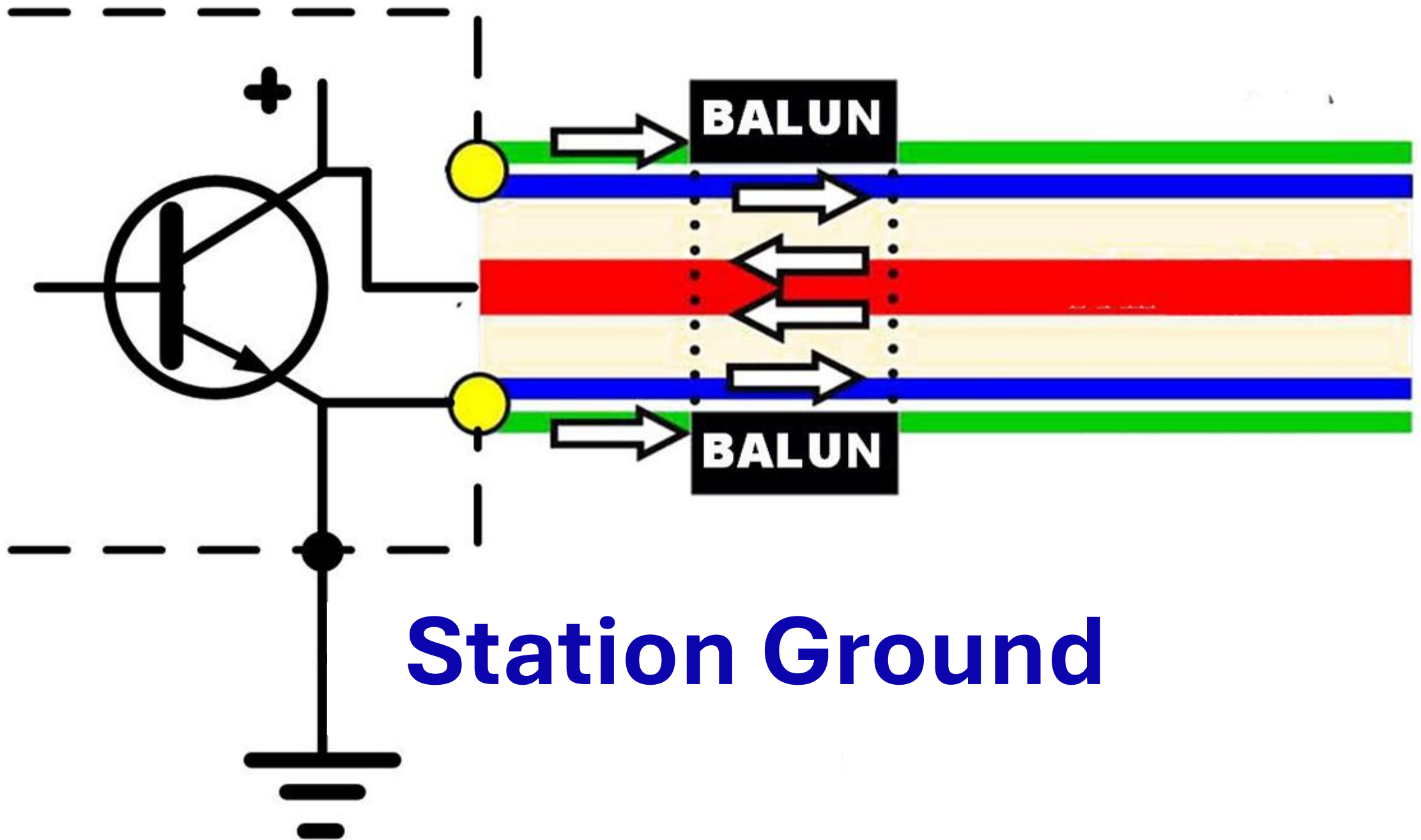**Why we may
have gotten away
without choking
in the shack?**





Experiment #144

The Myth of the RF Ground

Sooner or later, just about every ham who builds an HF station — whether it's at home, in the car, at Field Day, or for portable operation — experiences the rite of passage called an *RF burn*. Although painful, it rarely creates a physical mark, just a certain wariness on the part of the burn-ee. What's happening here?

You just had an exciting encounter with a high-impedance point on your antenna system. Impedance being the ratio of voltage to current, when power is applied, a high RF voltage will be present at these points. Who says you can't feel RF? "But wait," you exclaim, "the antenna is up in the air and connected to the antenna tuner! I'm not touching my antenna system!"

Oh yes, you are! Unless your station is built inside an RF-tight metal enclosure or is otherwise isolated from the antenna and feed line, every coax shield, every enclosure,


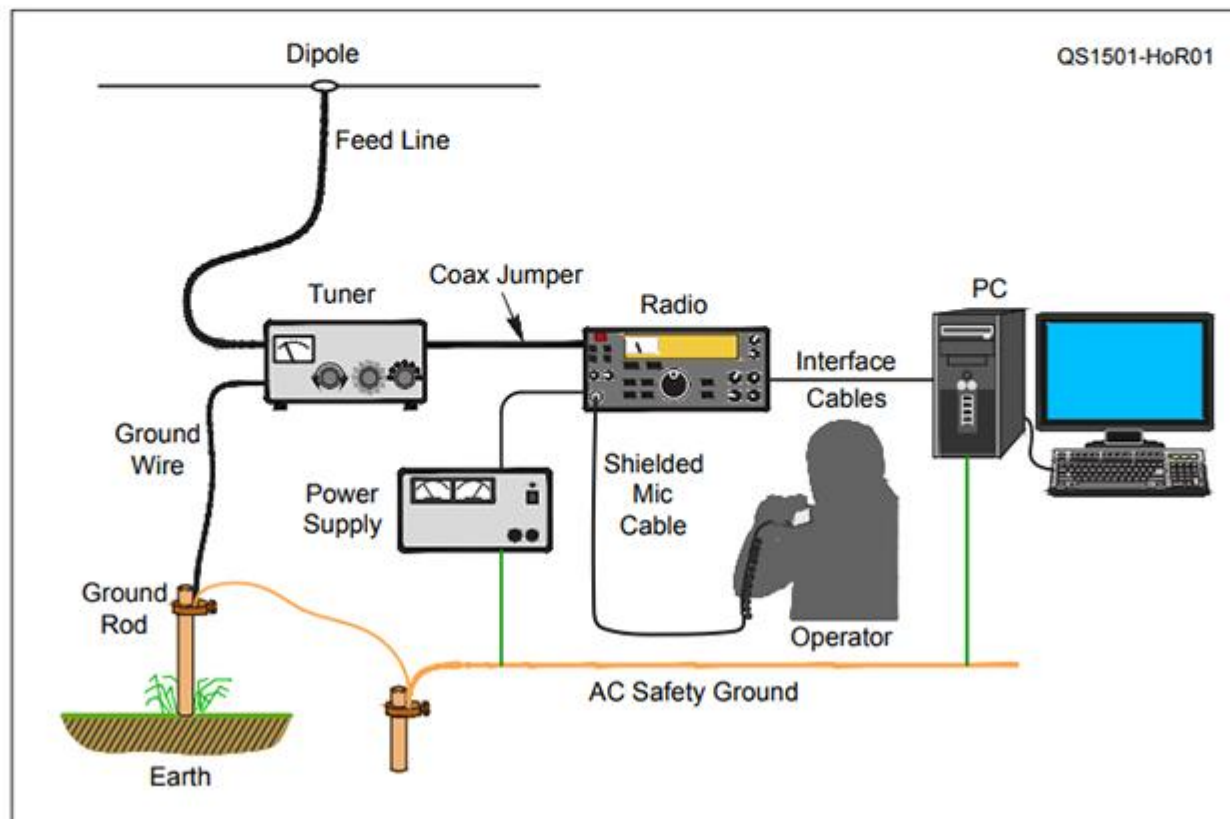


Figure 1 — The complete antenna system for a typical shack. Everything conductive, including the operator holding a microphone, is part of the antenna system.

**January
2015 QST
H. Ward
Silver**

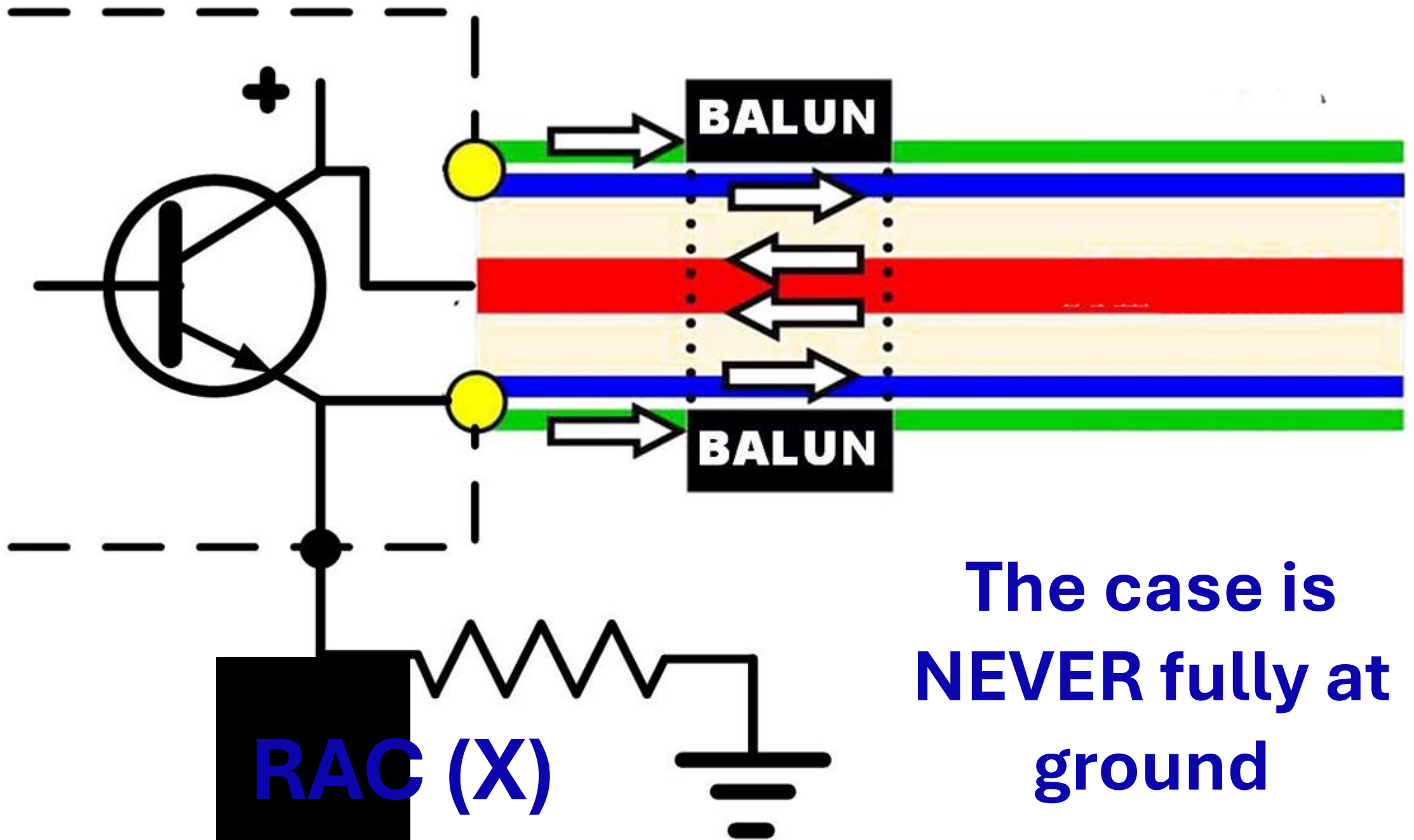**No Such
thing as a
“Perfect”
RF Ground**



The case is
NEVER fully at
ground

**Jim W6OEK's
experience with an
80-meter dipole with
a good balun**

Conductive Fabric Didn't Work



**Only shield current
chokes
in the shack did**

Ferrite Snap-On's



Mix 43/31 HF, 61 VHF/UHF

1 — 10m, dozen — 160m

Ferrite Sleeves



Ugly/Coax Balun



Toroid Balun



A Non-Double-Choked System is an RF Magnet

- **Your own feedlines not at 90°**
- **Other transmitters**
- **Other radio systems**
- **Atmospherics, QRN**


so

Choke, Choke, Choke

- **Transmitters**
- **Coaxes – TX & Antenna**
- **More than one balun OKAY**

Also with a 4:1 or 9:1

LDG

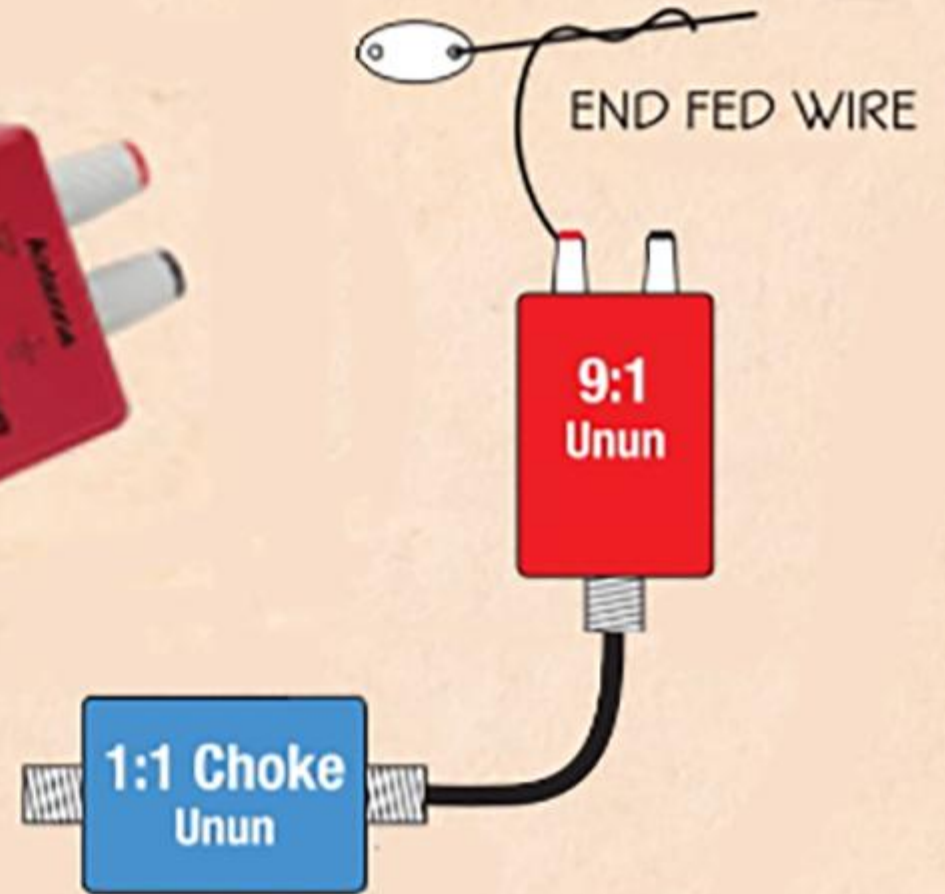



**w6nbcmail@
gmail.com**
w6nbc.com

DØGGY



"That's all Folks!"

